

Microvec

The Other Type of Video Display

Billy Garrett
POB 18806
Greensboro, NC 27419-8806

If you look closely at the video games in an arcade, you will see two main types of video displays. The "other" type of display is called a vector-graphics display (of course, the most common display is the raster type that operates like an ordinary television). The vector display is easily recognized because the displayed image is formed by line segments called vectors. The image resembles a stick figure or an engineering drawing. Because no low-cost vector displays are available commercially, I decided to design and build one for myself.

This article describes how the Microvec unit operates and how to build one. For less than \$225, you can have a complete, stand-alone vector-graphics controller that can produce

images like those in photos 1, 2, and 3. It will accept commands to draw lines with endpoints anywhere on a 256- by 256-element grid, and it can display any one of four "pages" of video information stored in memory. By connecting the controller to a common oscilloscope, you will have a vector-display unit that can be hooked to any computer. Interfaces specifically designed for use with the S-100 bus and the Radio Shack TRS-80 Model I computer are also described in this article.

The Arcade Syndrome

Whenever I finally tear myself away from a video-game arcade, I consider myself lucky to have any money left. By the time I arrive home, I'm ready to start designing my own video game. I have come to realize, however, that TRS-80 BASIC is too slow at handling graphics for my purposes; the only way to write an *interactive real-time* game that uses graphics extensively is to use machine language—a tedious process at best. Even worse is the limited resolution (128 by 48 picture elements) that the TRS-80 has to offer. Though other computers with higher resolution are available, I have found that the raster-scan display, as employed by all current home computers, can be difficult to use.

Raster Scan versus Vectors

A raster display is formed one line at a time, from the top of the screen

to the bottom (about 525 horizontal lines for a standard TV picture). In a high-resolution raster-scan display, the image is formed by turning on many small dots, called pixels (picture elements). Because so many pixels are in a small area, the eye blurs them into what appears to be a solid form. Many raster-scan displays are available for personal computing use, and the price depends on the type and resolution of the display desired. Even though raster-scan displays are widely used, they are not ideally suited for *all* display applications.

In a vector-display system, an image on the screen is made up of individual *line segments*, rather than dots. A display of this nature is commonly found in an arcade as part of a game. This kind of display is also used to produce schematics, structural outlines of a building, and can even be used for the complicated task of real-time aircraft simulation. Its main advantage over the raster-scan technique is simplicity of use: only two points must be known in order to draw a line; in a raster-scan device, the line is composed of many pixels, each of which must be kept track of individually and turned on or off.

With a vector display, the host processor only needs to send the starting and ending points of a line, which leaves the host processor with much more free time. Rapid animation can be achieved through the use of a vector-graphics display by employing this extra computing time.

Behind the Screens

Billy Garrett began work on the Microvec project as a junior at the University of South Carolina; the Engineering Department there was very helpful, and special thanks goes to Dr. Robert Pettes and Dr. Bill Eccles for their support and encouragement. The South Carolina Honors College, led by Dr. Mould, helped with the manuscript and photos. Due to the aid of Dr. Wierzba and Dr. Walters, work on the project achieved recognition at the IEEE's Region 3 Student Paper Contest, where it took third place. Norman McEntire encouraged the author to send the paper to BYTE in the form of a construction article. The photos in this article are by Howard Rhinehart.

The Problems of a Vector-Graphics Display

The major drawbacks to designing a vector display are twofold. The first problem is refreshing the display in sufficiently short time intervals to prevent the vectors from flickering. The solution to this problem is the use of a dedicated microprocessor built on the same board as the vector-display controller to handle the refresh and I/O (input/output) operations. An alternate solution to this problem would have involved the use of discrete integrated circuits or DMA (direct memory access) techniques; this increases the complexity of the circuit greatly, nearly doubling the number of parts required by the dedicated microprocessor approach.

The second problem is that the display used is not like a normal television. Instead, a vector-graphics generator needs an *x-y*-type display. Fortunately, a low-grade oscilloscope can be used, but it must have a *z*-axis input that will either blank or intensify the display. (I had an old Heathkit scope that was just sitting idle; it serves as a fine display for the controller described here.) The bandwidth of the scope is not critical. As long as each channel is rated for 100 kHz or more and both channels are DC-coupled, it should work fine.

General Overview

The basic outline of the Microvec unit is shown in the block diagram in figure 1. The microprocessor is responsible for sending coordinates of every vector's endpoints to the D/A (digital-to-analog) converters. Coordinates of the beginning point are

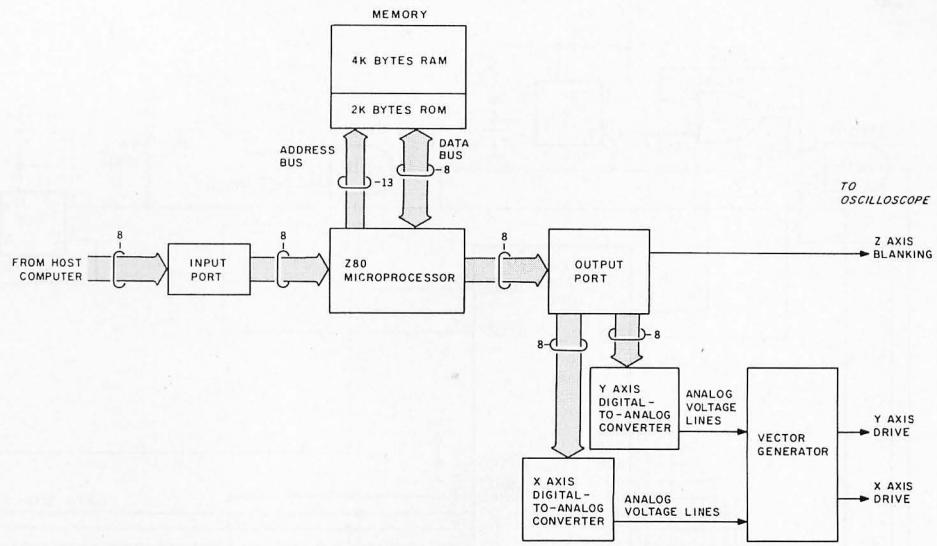


Figure 1: Block diagram of Microvec. The Z80 microprocessor accepts commands from a host computer system in the form of endpoint coordinates for vectors to be drawn, and transfers them periodically to digital-to-analog converters that drive vector-generating circuitry.

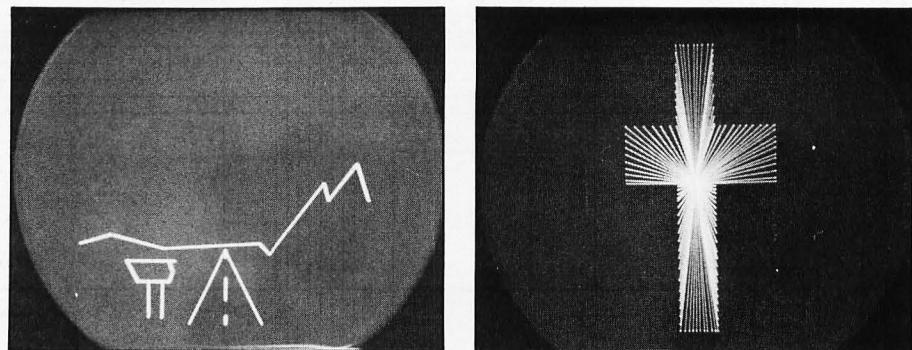


Photo 1: Images produced by Microvec. These two photos are freehand "doodles" drawn by the author with a TRS-80 Level II BASIC program. The combination of a host computer and the vector controller's dedicated Z80 makes a very flexible and powerful system.

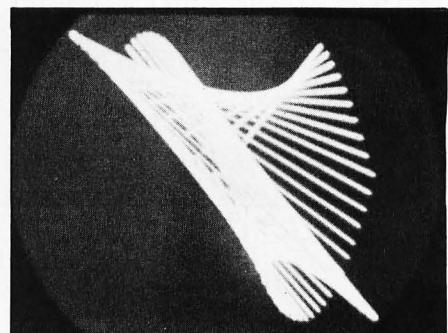
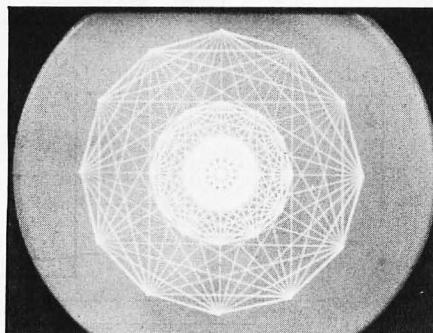
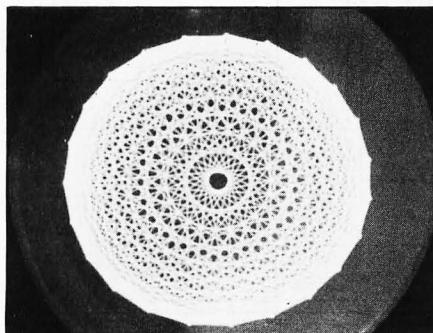


Photo 2: Circle-forms produced by the LCIRCLE program. These images were designed by simply specifying different parameters before running LCIRCLE. (See listing 2.)

Photo 3: An image drawn by the STICKS program. This is a vector-scan version of a program commonly used to demonstrate the high-resolution mode of Apple II computers. (See listing 4.)

(2a)

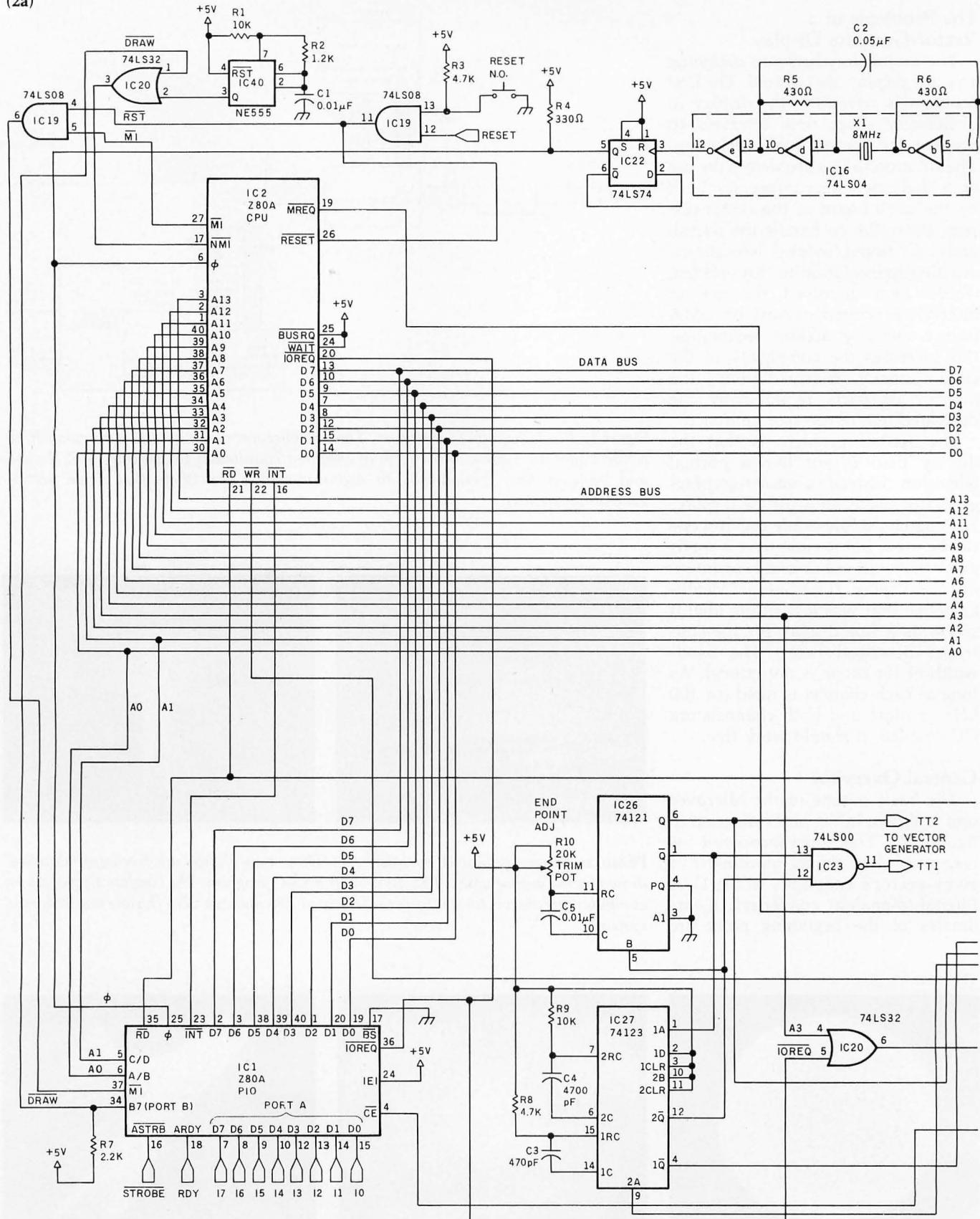


Figure 2: Schematic diagram of the Microvec system. Figure 2a, the main part of the system, contains the microprocessor, memory, D/A converters (digital-to-analog converters), and vector-generating circuitry. The microprocessor refreshes the display by repeatedly sending all the coordinates in the current memory page to the D/A converters. (Four pages of memory are on board; each can contain 255 vectors.) When the first part of a vector's coordinate is sent to the D/A converters, a voltage is produced that is represen-

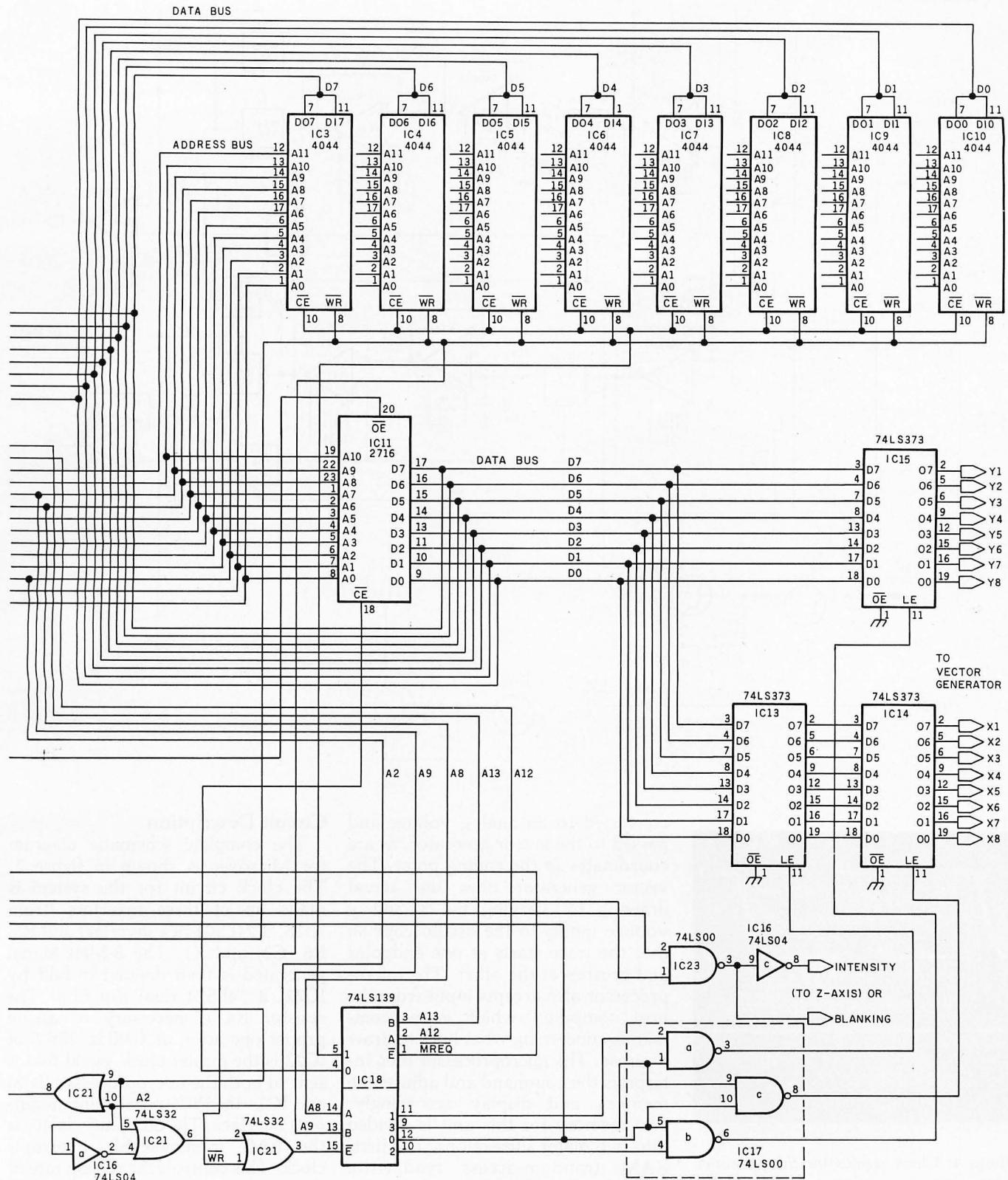


Figure 2a continued on page 512

tative of the starting point of the vector. A series of capacitors is charged to this voltage through a set of CMOS transmission gates. When the second part of the vector's coordinates is presented to the D/A converters, their output voltage becomes representative of the endpoint of the vector, and the voltage on the capacitors changes to this new value. The state of the transmission gates is changed so that the changing voltage on the capacitors is used to drive the display device (an oscilloscope).

(Figure 2a continued)


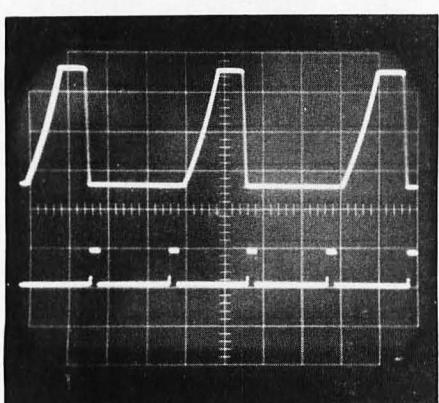
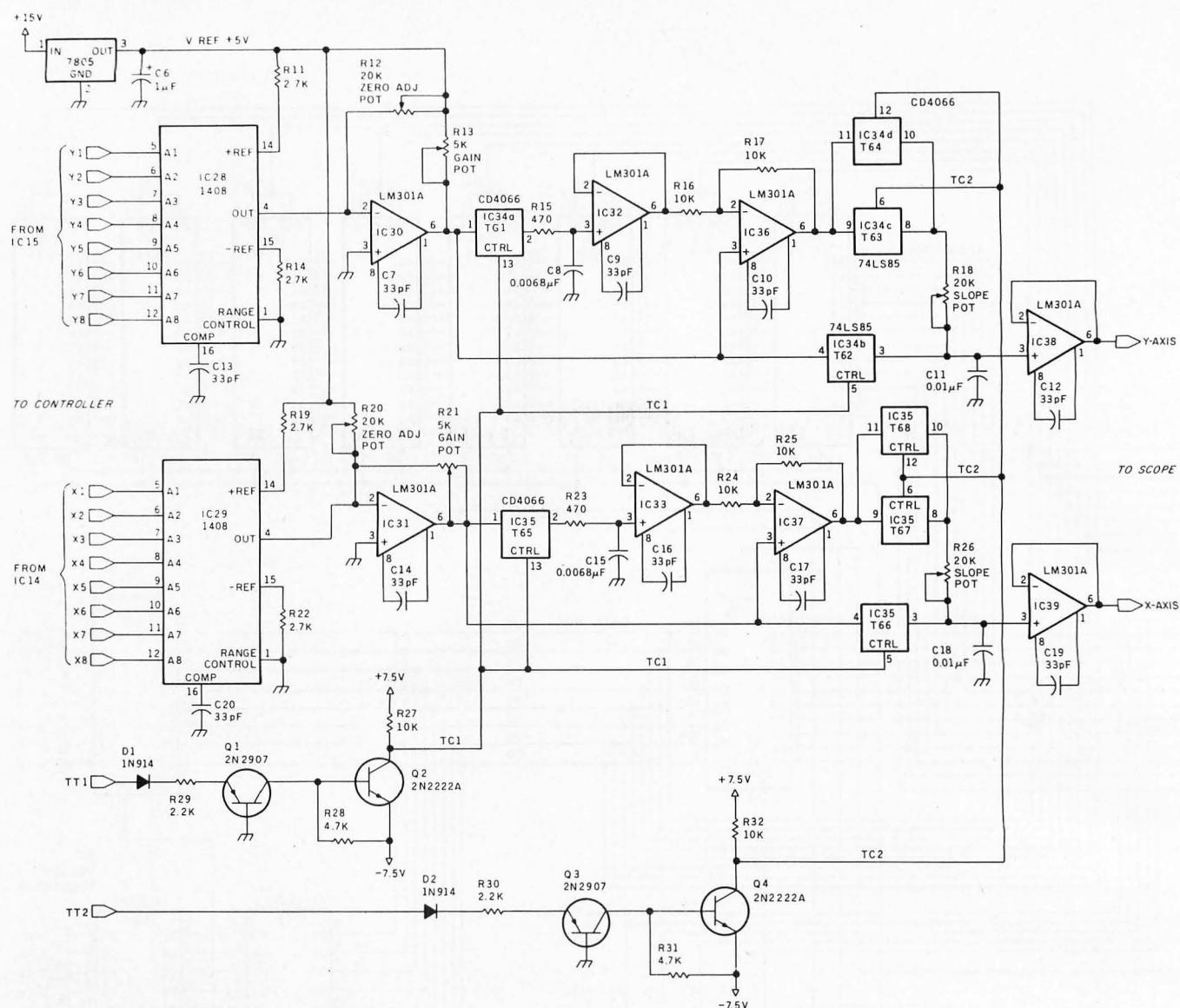


Photo 4: Clock signals for the Microvec system. The upper trace is the 4-HMz system clock; the lower trace is the adjustable refresh clock. The refresh clock determines how the processor divides its time between refreshing the screen and processing the host computer's commands.

converted to an analog voltage and passed to the vector generator, as are coordinates of the ending point. The vector generator does the actual drawing by varying the x and y voltage inputs to the oscilloscope so that the trace starts at one endpoint and finishes at the other. The microprocessor also accepts input from the host computer, which issues commands concerning what lines to draw or erase. The microprocessor then interprets the command and adjusts the memory and display accordingly. The memory for this unit is divided into two major subsections. The first, RAM (random-access read/write memory), is a place where the microprocessor stores coordinates for the lines to be drawn. The other type is EPROM (erasable programmable read-only memory), in which the microprocessor's control program resides.

Circuit Description

The complete schematic diagram for Microvec is shown in figure 2. The clock circuit for the system is made up of three inverters (from IC16, a 74LS04 hex inverter) and R5, R6, C2, and X1. The 8-MHz signal generated is then divided in half by IC22, a 74LS74 dual flip/flop. The resistor R4 is necessary to assure proper operation at 4 MHz. Pin 5 of IC22 is the master clock signal that is sent to both the microprocessor (IC2) and IC1, the PIO (parallel input/output) interface. The 555 timer, IC40, is the NMI (nonmaskable interrupt) clock. This controls the refresh rate of the display. At the 4-MHz system clock speed, a good refresh rate is obtained if R1 is 10 k Ω . See photo 4 for a look at this signal. The value of R1 may be decreased, but this will degrade the speed of the I/O operations. (In fact, if R1 is set too low, the

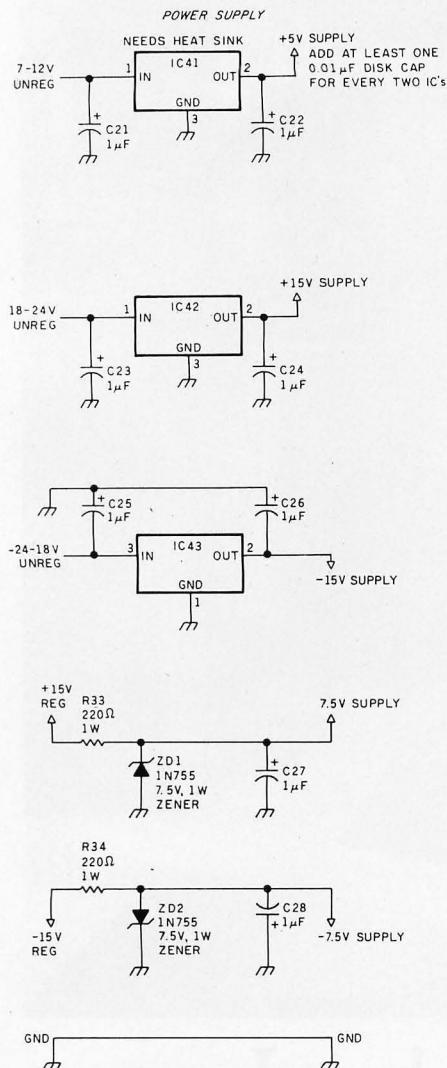

Number	Type	Gnd	+5V	+15V	-15V	+7.5V	-7.5V
IC1	Z80A-PIO	11	26				
IC2	Z80A-CPU	29	11				
IC3	4044	9	18				
IC4	4044	9	18				
IC5	4044	9	18				
IC6	4044	9	18				
IC7	4044	9	18				
IC8	4044	9	18				
IC9	4044	9	18				
IC10	4044	9	18				
IC11	2716	12	21,24				
IC12	74LS240	10	20				
IC13	74LS373	10	20				
IC14	74LS373	10	20				
IC15	74LS373	10	20				
IC16	74LS04	7	14				
IC17	74LS00	7	14				
IC18	74LS139	8	16				
IC19	74LS08	7	14				
IC20	74LS32	7	14				
IC21	74LS32	7	14				
IC22	74LS74	7	14				
IC23	74LS00	7	14				
IC24	74LS85	8	16				
IC25	74LS85	8	16				
IC26	74121	7	14				
IC27	74123	8	16				
IC28	1408	2	13	3			
IC29	1408	2	13	3			
IC30	LM301A	7	4				
IC31	LM301A	7	4				
IC32	LM301A	7	4				
IC33	LM301A	7	4				
IC34	CD4066			14	7		
IC35	CD4066			14	7		
IC36	LM301A	7	4				
IC37	LM301A	7	4				
IC38	LM301A	7	4				
IC39	LM301A	7	4				
IC40	NE555	1	8				

Figure 2b gives the specifics of power-supply filtering (be sure to see the power-supply connection table accompanying this figure).

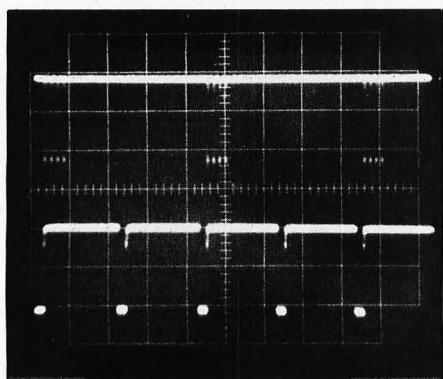


Photo 5: Timing signals that operate the vector-generating portion of the circuit. The lower trace is the 4-MHz system clock; the upper trace shows the strobe signals sent to the enable pin of IC18, a decoder. The decoder provides four separate, properly timed signals to operate the latches and transmission gates that make up the vector generator.

microprocessor will spend almost all its time doing video refresh, and the unit will be very sluggish in responding to commands.)

The microprocessor does have some control over the NMI requests. By raising pin 34 of IC1 high, the microprocessor can override the NMIs. This is essential to reset the system. The pins not shown for IC1 are part of "port B" and are not used in this design; therefore, they should be left disconnected. (Any other pins not shown are not used and should also be left alone.)


The memory, IC3 through IC11, is connected to the address bus. Each of these 4044 static memories is connected to one data line. Half of IC18, a dual 1-of-4 decoder, is used to select either the ROM (read-only memory) or the RAM.

The other half of IC18 decodes the strobes that are used to "fire" the vector generator. See photo 5 for a look at the enable signal on pin 15 of IC18. These four pulses are decoded by IC18 and are used to load and fire the vector generator. First, pin 9 of IC18 will pulse low, followed by pin 10, pin 11, and pin 12, in that order. This causes the proper bytes of data to be loaded into IC13, IC14, and IC15 (all are 74LS373 8-bit latches) and then sent on to the D/A converters. IC26 and IC27 (both are types of one-shots) handle the timing for the vector generator and are triggered by the last strobe, from pin 12 of IC18.

Because the x and y channels of the vector-generator circuitry are built identically, just the y-axis part of the circuit will be described. IC15 is connected to the D/A converter, IC28.

(2c)

(2d)

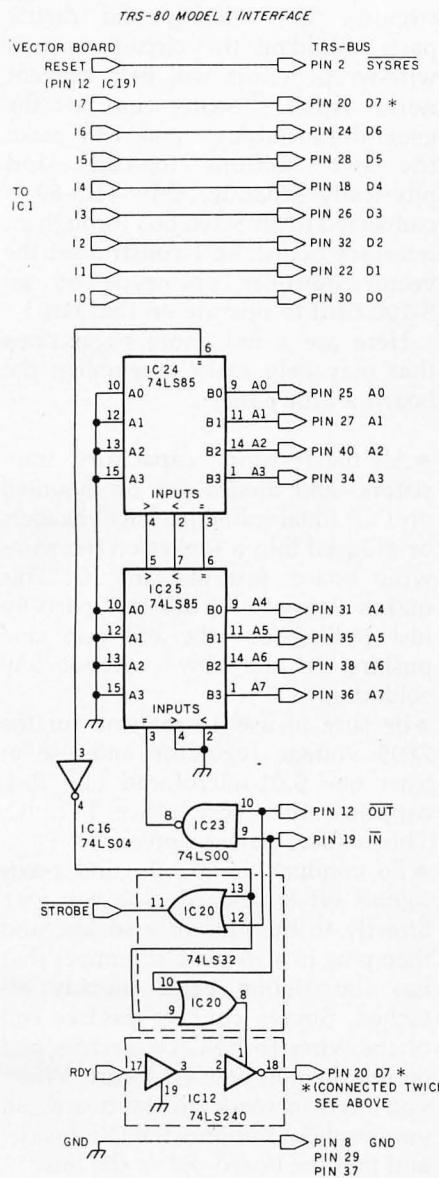

Figures 2c and 2d are interfaces to the Radio Shack TRS-80 Model I and the S-100 bus, respectively.

The signal out of pin 4 is a current that is proportional to the input value on pins 5 through 12. The op amp, IC30, converts this current into a voltage that should range over about ± 1 volt (V), depending on the gain adjustment, R13. The zero-adjustment potentiometer, R12, is used to set the midpoint of the D/A converter to 0 V. IC34 is a CMOS (complementary metal-oxide semiconductor) 4066 bilateral switch, sometimes called a TG (transmission gate). When its control input (i.e., pin 13) is at 7.5 V, it acts like a switch that has a contact resistance of about 80 ohms; however, when the control pin is at -7.5

V, its resistance is about 1 teraohm ($10^{12} \Omega$), which is a fairly good disconnection! The two signals that control the TGs, TC1 and TC2, are shown in photo 6. Note that these signals are affected by the endpoint-adjustment potentiometer, R10. Therefore, the signals in your circuit will look like that but will not necessarily have exactly the same timing. The four transistors and the parts around them are necessary to translate the TTL-level signals from the one-shots into CMOS levels for use by IC34 and IC35.

Basically, drawing a line occurs through the following sequence of

S-100 BUS INTERFACE

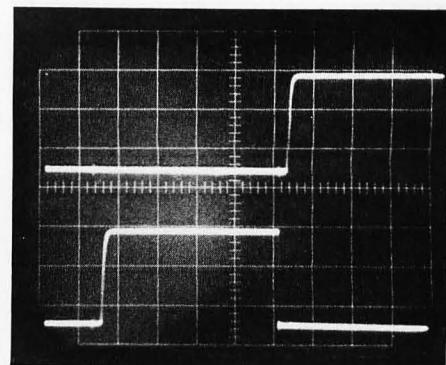
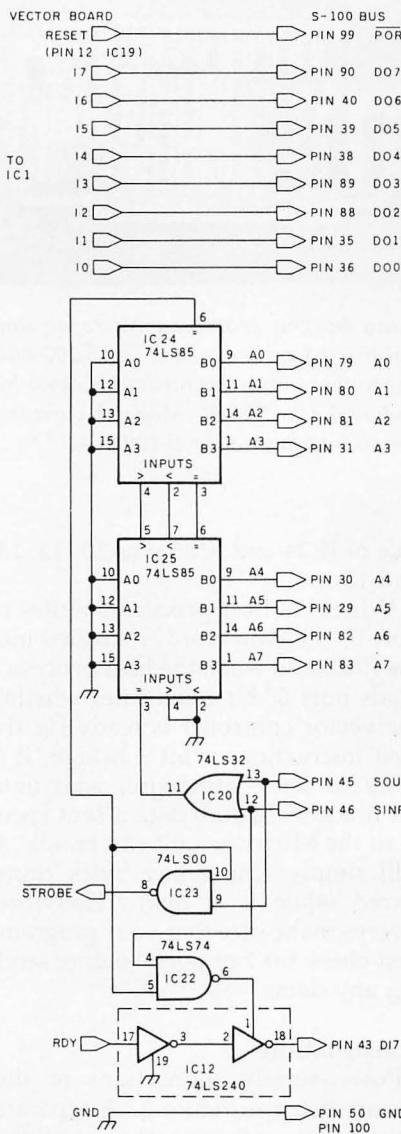


Photo 6: Translated signals that operate the transmission gates.

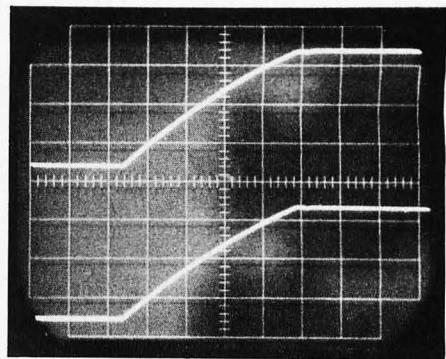


Photo 7: Output voltages that drive the oscilloscope. The starting and ending points for these "ramps" are determined by the output of the digital-to-analog converters.

events. First, both D/A converters are given a byte representing the starting point of a line, and their outputs are given a chance to settle. While in this state, TGs 1, 2, 5, and 6 are on, and the other TGs are off. This allows C8, C11, C15, and C18 to charge up to the voltage produced by the corresponding D/A converter. Next, all the TGs are turned off for about 12 microseconds (μ s). (Exact timing is determined by IC27, C4, and R9.)

The D/A converters are given the endpoint values and allowed to settle for 12 μ s. Then, TGs 3, 4, 7, and 8 are turned on for between 50 and 90 μ s (depending upon the endpoint-adjustment setting of R10). During this time, C11 and C18 either charge (if the final value is higher than the initial value) or discharge (if the final value is the lower). The result is that the output voltage takes some time to go from the value stored in the capacitors to the value being generated by the D/A converters. This produces a "ramp" waveform, as shown in photo 7.

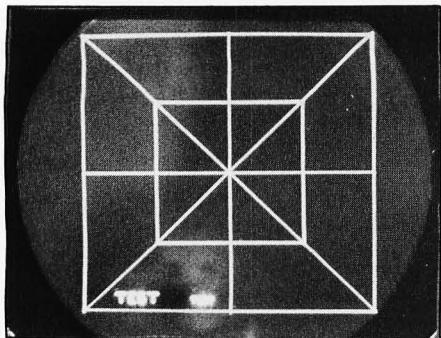


Photo 8: The built-in test and alignment pattern. Microvec automatically stores these vectors in memory whenever it is turned on, reset, or when the TEST command is given.

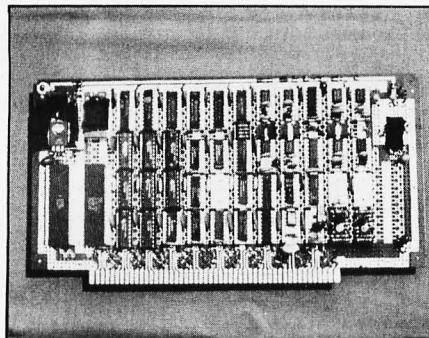


Photo 9: The prototype Microvec unit constructed on a card for the S-100 bus. The author chose this method because his Radio Shack TRS-80 Model I currently has an interface to the S-100 bus.

The charge rate is determined by the difference between the stored voltage and the final voltage. IC36 charges C11 through R18, and IC37 charges C18 through R26. Since the time constant (RC) of both sections must be equivalent, be sure C11 and C18 are very closely matched. The last op amp (IC38 and IC39) is used to buffer the output so that the scope will not affect the charging of C11 or C18.

Note in the photo that the outputs are not linear ramps. Instead, the capacitors charge in an exponential fashion (but since they both charge exponentially and have the same time constant, the display seems to produce straight lines). Only the most observant person is going to notice that the lines appear brighter toward the end of the line segment. Much more noticeable is that short vectors are brighter than longer vectors; this is because each vector is "on" for exactly the same length of time. That is why the letters in the words "TEST" in photo 8 are much brighter than the segments of the box. Although this is somewhat annoying, it is easy to get used to.

The power-supply regulators and zener diodes are connected in a normal way, as is shown in figure 2b. The two different host-computer interfaces are also quite simple. The data bus is attached to the "port A" inputs of the PIO, IC1. The lower 8 bits of the address bus are monitored by IC24 and IC25 (see figure 2c and figure 2d); the ICs are set up to enable I/O when the host addresses port 0. (If you want to change this address, simply alter the pattern on the "A"

side of IC24 and IC25 pins 10, 12, 13, and 15.)

When the host processor writes to port 0, the data word is strobed into the PIO; and when the host processor reads port 0, bit 7 indicates whether the vector controller is ready for the next instruction. If bit 7 is high, it is okay to send; otherwise, wait until the line goes high. If data is sent faster than the Microvec unit can handle, it will simply ignore any bytes transferred while it is busy. Therefore, always make sure that your programs first check bit 7 of port 0 before sending any data.

Construction

Power-supply connections to the ICs are listed in figure 2. A separate listing of the other parts is provided in the text box "A Shopping List" on page 519. Make a photocopy of the schematic and as you attach each wire, check it off. That way, if you are interrupted or need to leave the board for a while, you will know where you are when you return. You will find that if you are not careful in the building phase, you will spend a great amount of your time tracking down wiring errors; thus, as a word to the wise, go slowly and double-check every wire. Note that the D/A converters have an unusual arrangement of their address pins in that A1 is the *most* significant bit rather than the *least* significant bit. Make sure that you connect the lines as shown.

As you can see from photo 9, the prototype is constructed on an S-100 wire-wrap board. If you do not plan to install your board in an S-100 system, I recommend that you use

two separate boards and divide the circuitry into analog and digital parts. Building the circuit on two wire-wrap boards will help prevent noise from showing up in the generator's outputs and will make the two sections logically and physically separate. (My TRS-80 is connected to an S-100 bus through an interface board, so I constructed the vector-controller prototype on an S-100 card to operate on that bus.)

Here are a few more suggestions that may help make assembling the board a little easier:

- All the resistors, capacitors, transistors, and diodes can be mounted on DIP (dual-inline package) headers or plugged into a socket on the wire-wrap board, just like any IC. This makes it easy to try different parts by just pulling out the old part and pushing in the new—without any soldering.
- Be sure to use a heat sink for the 7805 voltage regulator and use at least one 0.01-microfarad (μ F) disk capacitor for every other TTL IC. This reduces power ripple.
- To conduct the *x*-, *y*-, and *z*-axis signals off the board, you can wire directly to the pins of a socket, and then plug in a 16-pin DIP jumper that has flat ribbon cable already attached. Simply connect the free end of the wires to BNC connectors and mount them in your enclosure. When you need to work on the board, all you need do is unplug the DIP header and pull the board out of the bus.
- Note that both blanking and intensify signals are provided, although only one will be needed.

Make sure that you buy Z80A 4-MHz-rated parts. At the time of this writing, no 2716 EPROM is rated for 4 MHz, but a 2716-1 has a 350-nanosecond (ns) access time and should work fine. After I built my board, I substituted parts rated at 2.5 MHz, and they seemed to work fine at the 4-MHz rate; but there is no guarantee that this will be the case for all 2.5-MHz parts over even a narrow temperature range.

Software

The program I have written to drive Microvec's Z80 divides the available memory into 255-vector "pages." This allows the user to display or work on any of the four

pages independently. In this arrangement, the available memory is almost completely used. The memory for storing vectors could easily be expanded to 62 pages; however, that many extra pages would force the design to occupy several boards. Any one of the four different pages can be displayed while the user is editing that page (or any other page). This leaves at least two pages for storage.

Editing functions include commands for adding a new vector, deleting a given vector, clearing the entire page, deleting the last vector, and much more. See table 1 for a summary of the commands.

Figure 3 is a representation of the points available on the screen. If you want to draw a line across the bottom of the screen, you would need to send the following sequence of bytes: 4,0,0,255,0 (the first byte is the command—in this case, draw a line; the following 4 bytes give the starting point [0,0] and the ending point [255,0]). To erase that line, you could send the command 5,0,0,255,0; or you could simply send the command to delete the last vector: 6. This would have turned off the one line that was lit.

The commands DRAW, UNDRAW, CLEAR, and DELETE affect the MPAGE, which is the page you are editing. Use the command MODP to change the page number you want to work in. Initially, MPAGE is set to page 0. Use the command DISP to select DPAGE, the page you want displayed. DPAGE is initially set to 0. If you draw a line on one page and are displaying another, the displayed image will not change. The only way to watch the unit add or delete vectors is to set MPAGE and DPAGE to the same number.

The command TEST is the only command, other than RST, that will affect the display even if MPAGE and DPAGE are not the same. It produces the image in photo 8 by putting the vectors in memory; it does not reset the unit. The RST command does, however, reset the unit. Whenever Microvec is turned on, or reset to its initial state, it automatically performs a TEST command. Thus, the effect of RST is to both reset and test the unit. It takes a special command sequence to accomplish the RST function: 0,0,0,0,7,15. The "15" is a simple form of insurance; should a "7" code be sent accidentally, nothing will

A Shopping List

As a help, here is a condensed shopping list of necessary parts. The prices shown in this list are approximate and representative of parts available through mail-order ads in various issues of BYTE. Since this article was written, the prices will almost certainly have gone down on some of the parts.

The only hard-to-get part is the programmed EPROM. If you are lucky enough to have an EPROM programmer, you can "burn" the program into the EPROM yourself. If you want a 2716 programmed, there is a charge of \$10 to copy the program on each 2716 (no other type EPROM), which must be erased. You will receive the latest version of the program. However, there is no guarantee expressed or implied. Additionally, a disk is available with all the programs in this article, plus several other programs and the source code to the EPROM, for \$15. Send a check or money order (including \$2 for postage and handling) to Garco, POB 18806, Greensboro, NC 27419-8806. If you order a copy of either the EPROM or the disk, you'll also receive any errata sheets and additional documentation. Because I'm also planning on providing a revised EPROM, I need to know how many people would be interested. Those that send in an order will be on a mailing list. This offer is subject to change at any time.

Quantity	Part	Amount
1	Z80A-CPU	\$10.50
1	Z80A-PIO	8.60
8	4044 RAMs	31.92
1	2716-1 Preprogrammed	26.00
1	74LS240 Octal TS Inverter	1.65
3	74LS373 Octal Latches	4.35
1	74LS04 Hex Inverter	0.25
2	74LS00 Quad Nand Gates	0.50
1	74LS139 Dual 2-4 Decoder	0.75
1	74LS08 Quad And Gate	0.35
2	74LS32 Quad Or Gates	0.70
1	74LS74 Dual Flip/Flop	0.45
2	74LS85 4-Bit Comparators	2.30
1	74121 One-Shot	0.29
1	74123 Dual One-Shot	0.55
2	MC1408L8 8-Bit D/A Converters	11.90
8	LM301A Op Amps	3.12
2	4066 Quad Bilateral Switches	1.50
1	555 Timer	0.39
1	7805 5-Volt Regulator	0.89
1	78L05 Low-Power 5-Volt Regulator	0.79
1	7815 15-Volt Regulator	0.99
1	7915 -15-Volt Regulator	1.19
25	16-Pin WW Gold Sockets	17.25
4	20-Pin WW Gold Sockets	4.39
8	18-Pin WW Gold Sockets	7.92
2	40-Pin WW Gold Sockets	3.98
1	24-Pin WW Gold Socket	1.45
1	Vector WW Board 8800V DP	22.20
1	Reset Switch	1.50
1	8-MHz Crystal	1.99
27	Assorted Resistors	2.70
7	10-Turn Potentiometers	14.00
28	Assorted Capacitors	10.00
4	Transistors	2.00
2	1N914 Diodes	1.00
2	7.5-V 1-W Zener Diodes	1.00
1	16-Pin Jumper Cable (18-inch)	5.40
20	Despiking Caps (0.1 μ F)	5.30
1	Heat Sink	0.75
1	Wire-Wrap Wire	9.95
		Total: \$222.71

Code	Number of Bytes	Command Summary	
		Name	Description
1	2	MODP	Modify page (MPAGE)
2	2	DISP	Display page (DPAGE)
3	1	CLEAR	Clear MPAGE
4	5	DRAW	Draw line in MPAGE
5	5	UNDRAW	Erase line in MPAGE
6	1	DEL	Delete last vector in MPAGE
7	2	RST	Reset if key is correct
8	1	TEST	Turn on test pattern

Table 1: Summary of the commands to Microvec. The host system uses these commands to control the display of the four memory pages. In the table, MPAGE is the page being modified, while DPAGE is the page being displayed.

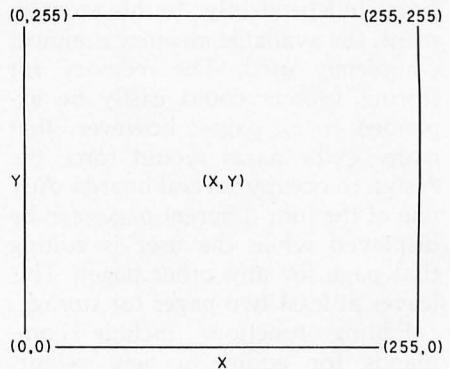


Figure 3: Representation of the oscilloscope display screen. Microvec can draw vectors with endpoints at any of the coordinates shown.

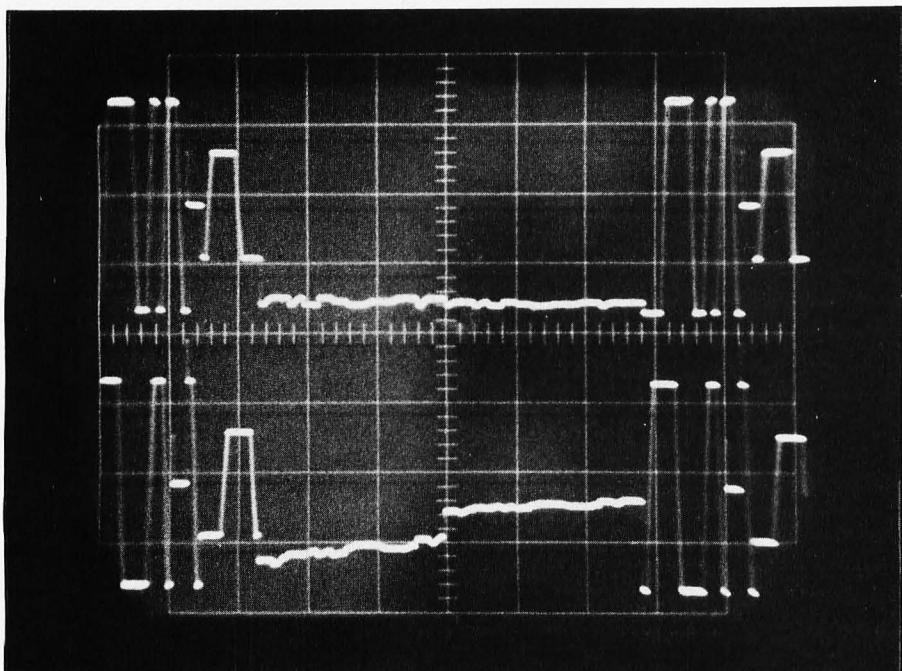


Photo 10: Comparison of the x- and y-axis driving signals while Microvec is displaying the test pattern of photo 8.

Listing 1: Controlling software for Microvec's Z80 processor. This assembly-language program is stored in an EPROM installed on the Microvec circuit card; it allows the Z80 microprocessor to display vectors stored in memory and to accept commands from a host computer system.

```

3
4
5
6
7
8
9
10
11      0000'
12
13
14
15
16
17
18
;
***** Copyright (C) 1981 By Billy Garrett *****
***** MICROVEC V1.0 *****
***** Vector Graphics Generator Program MICROVEC V1.0
      ASBG      ;Force the assembly at location 0 H
      ORG 0000H ;Start
              ;Startup routine
;
;COMMENT ^
This is a model of the registers inside of the Z80 and
how they are used by this program. There are some registers
that have dedicated functions, and their contents must not

```

Listing 1 continued on page 521

happen to all your hard work. The "15" is just a key.

Almost any command you can imagine might be added to the Z80 controller program simply by altering the code in the EPROM. Currently, the program occupies about 800 bytes of the 2048 bytes available. This leaves plenty of room. The assembled program is shown in listing 1.

The program is highly dependent on the interrupt structure of the Z80. Simply stated, two types of interrupts are available to Z80 programmers: the highest priority one is the NMI. Whenever the NMI signal is active, and as soon as the processor finishes the current instruction, the interrupt is acknowledged. The address 66 hexadecimal is placed in the program counter; the program at this location causes the system to draw a line. The important point is that the processor is being interrupted about 10,000 times each second, so that even when the host system is not sending commands to the board, half the Z80's time is being used to redraw the display.

The second type of interrupt is called simply INT. It is used when the host system has information to transfer to Microvec. Because this signal can be "masked" by the Z80, the processor can be programmed to ignore or postpone it.

Calibration

Before installing any ICs, check the output of each voltage regulator. Make sure that their outputs are within 5 percent of their rated values. Then, turn the power off and adjust R12 and R20 to about 5 kΩ. Next, adjust R13 and R21 to about 2 kΩ. After

Text continued on page 527

Listing 1 continued:

Listing 1 continued:		
150 009D F1 C3 00A5	POP AF JP SKTP	Restore AF ;Skip first inwait, already done
151 009E	;	;
152	;	;
153	;	;
154	POP AF JP INWAIT	;Wait on input ;Set carry flag
155	SCF	;Enable interrupts
156	..0001: JR C,..0001	;Wait on interrupt
157	DE,JIATBL	;Load DE with JTABLE base address
158	AND 7FH	;Make sure the value is positive
159	DE,JIATBL	;Is the command greater than NUMCOM?
160	CP P,INPNT	;If out of range, go back to input
161	JP P,INPNT	;
162	ADD A,A	Shift A right
163	ADD A,E	;
164	LD E,A	Add the offset
165	LD A,(DE)	;
166	LD A,(DE)	Put it back
167	INC DE	;Load A indirect
168	LD A,(DE)	Put low byte in L
169	LD H,A	Point to next byte
170	JP (HL)	;Load A indirect again
		;Put the high byte in H
		;Jump indirect
		Clear Current MPAGE
		229
		010B
		230
		010C
		224
		010F
		225
		010E
		226
		0104
		227
		0106
		228
		0108
		Clear Current MPAGE
		229
		010B
		230
		010C
		224
		010F
		232
		0105
		233
		0110
		234
		0111
		235
		0112
		236
		0113
		237
		0114
		238
		0115
		239
		0116
		240
		0118
		32 1004
		241
		011B
		DD E5
		242
		011D
		FD E1
		243
		011F
		C3 COA1
		Draw New Vector Command
		244
		0122
		79
		21 1000
		245
		0123
		85
		246
		0126
		85
		247
		0127
		6F
		248
		0128
		7E
		249
		0129
		3C
		250
		012A
		C2 0140
		252
		012D
		57
		253
		012E
		FB
		254
		012F
		38 FE
		255
		0130
		256
		257
		0131
		37
		258
		0132
		FB
		259
		0133
		38 FE
		260
		0134
		37
		261
		0135
		37
		262
		0136
		38 FE
		263
		0137
		38 FE
		264
		0138
		37
		265
		013A
		FB
		266
		013B
		38 FE
		267
		013D
		C3 COA1
		Draw New Vector Command
		244
		0122
		79
		21 1000
		245
		0123
		85
		246
		0126
		85
		247
		0127
		6F
		248
		0128
		7E
		249
		0129
		3C
		250
		012A
		C2 0140
		252
		012D
		57
		253
		012E
		FB
		254
		012F
		38 FE
		255
		0130
		256
		257
		0131
		37
		258
		0132
		FB
		259
		0133
		38 FE
		260
		0134
		37
		261
		0135
		37
		262
		0136
		38 FE
		263
		0137
		38 FE
		264
		0138
		37
		265
		013A
		FB
		266
		013B
		38 FE
		267
		013D
		C3 COA1
		Draw New Vector Command
		244
		0122
		79
		21 1000
		245
		0123
		85
		246
		0126
		85
		247
		0127
		6F
		248
		0128
		7E
		249
		0129
		3C
		250
		012A
		C2 0140
		252
		012D
		57
		253
		012E
		FB
		254
		012F
		38 FE
		255
		0130
		256
		257
		0131
		37
		258
		0132
		FB
		259
		0133
		38 FE
		260
		0134
		37
		261
		0135
		37
		262
		0136
		38 FE
		263
		0137
		38 FE
		264
		0138
		37
		265
		013A
		FB
		266
		013B
		38 FE
		267
		013D
		C3 COA1
		Draw New Vector Command
		244
		0122
		79
		21 1000
		245
		0123
		85
		246
		0126
		85
		247
		0127
		6F
		248
		0128
		7E
		249
		0129
		3C
		250
		012A
		C2 0140
		252
		012D
		57
		253
		012E
		FB
		254
		012F
		38 FE
		255
		0130
		256
		257
		0131
		37
		258
		0132
		FB
		259
		0133
		38 FE
		260
		0134
		37
		261
		0135
		37
		262
		0136
		38 FE
		263
		0137
		38 FE
		264
		0138
		37
		265
		013A
		FB
		266
		013B
		38 FE
		267
		013D
		C3 COA1
		Draw New Vector Command
		244
		0122
		79
		21 1000
		245
		0123
		85
		246
		0126
		85
		247
		0127
		6F
		248
		0128
		7E
		249
		0129
		3C
		250
		012A
		C2 0140
		252
		012D
		57
		253
		012E
		FB
		254
		012F
		38 FE
		255
		0130
		256
		257
		0131
		37
		258
		0132
		FB
		259
		0133
		38 FE
		260
		0134
		37
		261
		0135
		37
		262
		0136
		38 FE
		263
		0137
		38 FE
		264
		0138
		37
		265
		013A
		FB
		266
		013B
		38 FE
		267
		013D
		C3 COA1
		Draw New Vector Command
		244
		0122
		79
		21 1000
		245
		0123
		85
		246
		0126
		85
		247
		0127
		6F
		248
		0128
		7E
		249
		0129
		3C
		250
		012A
		C2 0140
		252
		012D
		57
		253
		012E
		FB
		254
		012F
		38 FE
		255
		0130
		256
		257
		0131
		37
		258
		0132
		FB
		259
		0133
		38 FE
		260
		0134
		37
		261
		0135
		37
		262
		0136
		38 FE
		263
		0137
		38 FE
		264
		0138
		37
		265
		013A
		FB
		266
		013B
		38 FE
		267
		013D
		C

Listing 1 continued:

278	014A	FD 23	INC	IY	;	point to the next free space
279	014C	1D	DEC	E	;	Decrement count
280	014D	20 F4	JR	NZ,LOOP	;	Loop back
281	014F	72	LD	(HL),D	;	Now, increase the number of v
282	0150	78	LD	A,B	;	Load DPAGE in A
283	0151	B9	LD	C	;	Load DPAGE in C
284	0152	C2 00A1	CP	;	;	Is it MPAGE?
285	0155	7A	NZ,INPUT	A,D	;	If not, then done
286	0156	32 1004	LD	(NUMTEC),A	;	Otherwise, put the number in
287	0159	C3 00A1	LD	NUMTEC	;	NUMTEC
			JP	INPUT	;	Go back

Undraw Vector Command

Indraw Vector Command	Indraw Vector Command
<pre> 279 014C 1D F4 DEC NZ,LOOP ;Decrement count 280 014D 20 F4 DD (HL),D ;Loop back 281 014F 7F UNDRAW: LD HL,NUMVO ;Load HL with a base pointer 282 0150 78 ADD A,C ;Now, increase the number of vectors 283 0151 B9 CP A,B ;Load DPAGE in A 284 0152 C2 00A1 JP C ;Is it MPAGE? 285 0155 7A JP NZ,INPUT ;If not, then done 286 0156 32 1004 ID A,D ;Otherwise, put the number in A 287 0159 C3 00A1 ID (NUMVEC),A;Store in NUMVEC INPUT JP ;Go back </pre>	<pre> 288 015C 21 1000 SUBTBL Undraw Vector Command 289 015F 79 UNDRAW: LD HL,NUMVO ;Get the MPAGE number in A 290 0160 85 ADD A,L ;; 291 0161 6F ADD L,A ;; 292 0162 7E ADD A,(HL) ;Get the # of vectors in the MPAGE 293 0163 F5 PUSH AF ;Save it 294 0164 37 TBL WAIT: ;Wait on input 295 0165 38 FE ADD C,..0009 ;Enable interrupts 296 0166 38 FE ADD C,..0009 ;Wait on interrupt 297 0167 57 TBL D,A ;Put X1 in D 298 0168 57 TBL D,A ;Wait on input 299 0169 37 TBL H,A ;Set carry flag 300 0170 38 FE ADD C,..000B ;Enable interrupts 301 0171 67 TBL H,A ;Wait on interrupt 302 0172 38 FE ADD C,..000A ;Put Y1 in E 303 0173 5F TBL H,A ;Wait on input 304 0174 37 TBL D,A ;Set carry flag 305 0175 38 FE ADD C,..000C ;Enable interrupts 306 0176 6F TBL D,A ;Wait on input 307 0177 38 FE ADD C,..000B ;Set carry flag 308 0178 F1 ADD D,A ;Put Y2 in L 309 0179 60 ADD H,A ;Get AF back 310 017A 7E ADD H,A ;Check for any vectors in page 311 017B 37 TBL D,INPUT ;If not, go back 312 017C 38 FE ADD C,..000C ;Otherwise, save IX for later 313 017D 6F PUSH IX ;Save AF 314 017E 65 ADD A,(IX+0) ;Load A with first entry 315 017F 00 ADD CP D ;Is it the same as X1? 316 017G 00 ADD IX ;If so, jump to FIND1 317 017H 20 F5 ADD INC IX ;Increment IX by four 318 017I 0E ADD INC IX ;; 319 017J 23 ADD INC IX ;; 320 0180 F5 NOPFIND: PUSH AF ;Find out 321 0181 DD 7E C0 ADD LD A,(IX+1) ;Is the next entry Y1? 322 0182 BA 00 ADD CP E ;Find out 323 0183 00 ADD DEC A ;Decrement the counter 324 0184 DD 23 ADD JR NZ,NOPFIND ;Loop 325 0185 DD 23 ADD ADONE ;Go back if not found 326 0186 DD 23 ADD ;; 327 0187 DD 23 ADD ;; 328 0188 DD 23 ADD ;; 329 0190 20 F1 WELL: INC IX ;; 330 0191 20 ED INC IX ;; 331 0193 18 55 INC IX ;; 332 0195 DD 7E C1 F1ND1: LD A,(IX+1) ;Is the next entry Y1? 333 0196 BB F1 INC IX ;; 334 0198 00 F1 INC IX ;; 335 0199 20 F2 INC IX ;; 336 019A 00 F2 INC IX ;; 337 019B BC F1 INC IX ;; 338 019C 20 F6 INC IX ;; 339 01A1 DD 7E C3 INC IX ;; 340 01A4 BD F5 INC IX ;; 341 01A5 20 F0 INC IX ;; 342 01A7 F1 INC IX ;; 343 01A8 FD F5 INC IX ;; 344 01A9 E1 INC IX ;; 345 01A8 DD B5 INC IX ;; </pre>
<pre> 346 01AD DI DE ;Put it in DE 347 01AE 37 SCP ;Set the carry flag 348 01AF 3F CCP ;Subtract the end from the found loc. 349 01B0 ED 52 SBC HL,DE ;HL,DE 350 01B2 A,H SBC HL,DE ;HL,DE 351 01B3 CP OOH ;See if H is zero 352 01B5 NZ,NOPE ;Go to NOPE if it isn't 353 01B7 A,L SBC HL,DE ;HL,DE 354 01B8 CP OAH ;Correction factor 355 01BA Z,MOVE ;If zero, then don't move anything 356 01BC DEC HL,DE ;Decrease HL by four 357 01BD 2B DEC HL,DE ;HL,DE 358 01BE 2B DEC HL,DE ;HL,DE 359 01BF 2B DEC HL,DE ;HL,DE 360 01C0 C5 PUSH BC ;Keep BC for a while 361 01C1 E5 PUSH HL ;Push HL 362 01C2 C1 PUSH BC ;Byte count into BC 363 01C3 DD E5 PUSH HL ;Place where vector was found 364 01C5 E1 PUSH IX ;Put it in HL 365 01C6 25 POP HL ;Add four to HL 366 01C7 25 INC HL ;; 367 01C8 23 INC HL ;; 368 01C9 23 INC HL ;; 369 01CA DD E5 PUSH IX ;Put the found location 370 01CC D1 POP DE ;into the destination register 371 01CD ED BO LDIR ;Move the vectors smoothly in place 372 01CF C1 POP BC ;Restore BC 373 01D0 FD 2B NOMOVE: DEC IY ;And close up the end 374 01D2 FD 2B DEC IY ;; 375 01D4 FD 2B DEC IY ;; 376 01D6 FD 2B DEC IY ;; 377 01D8 79 ADD IY,A ;Load MPAGE into A 378 01D9 79 ADD HL,NUMVO ;Load HL with the base address 379 01DC 85 ADD A,L ;; 380 01DD 6F ADD IY,A ;; 381 01DE 7E ADD A,(HL) ;; 382 01E0 77 ADD (HL),A ;Get the offset 383 01E1 5F ADD E,A ;; 384 01E2 78 ADD A,B ;; 385 01E3 85 ADD IY,A ;; 386 01E4 20 04 ADD C,..000F ;Get the number of vectors into A 387 01E5 32 1004 ADD NZ,ADONE ;Decrease the # of vectors by one 388 01E6 01E7 ADD A,E ;;Save it back where it was found 389 01E7 32 1004 ADD (NUMVEC),A ;And place the new number in NUMVEC 390 01EA 01E8 ADD IX ;Restore IX to it's original value 391 01FC 39 ADONE: POP IY ;Go back </pre>	<pre> 392 01EF 79 SUBTBL Delete Command 393 01F0 85 ADD IY,A ;Get the MPAGE 394 01F1 85 ADD HL,NUMVO ;Get the base address 395 01F2 85 ADD A,L ;; 396 01F3 6F ADD L,A ;; 397 01F4 7E ADD A,(HL) ;; 398 01F5 7E ADD OOH ;Get the # of vectors 399 01F6 00 ADD IY,A ;; 400 01FB 2D ADD C,..000F ;Is it zero? 401 01FC 77 ADD IY,A ;; 402 01FD 57 ADD D,A ;; 403 01FE 79 ADD A,C ;; 404 01FF 85 ADD C,..000F ;; 405 0200 C2 0207 ADD NZ,DECR ;Compare to DPAGE 406 0203 7A ADD A,D ;Go back if not same 407 0204 32 1004 ADD (NUMVEC),A ;Get the # back 408 0205 DD 2B ADD IY,A ;And put in NUMVEC 409 0206 0209 DEC IY ;Decrease IY by four 410 0207 FD 2B DEC IY ;; 411 0208 FD 2B DEC IY ;; 412 0209 FD 2B DEC IY ;; 413 0210 C3 00A1 INPUT JP ;Go back </pre>
<pre> Delete Command </pre>	<pre> Delete Command </pre>

November 1982 © BYTE Publications Inc 523

Listing 1 continued:

```

413      0212    37      FB      38 FE    FE OF    CA 0000  C3 00A1
414      0212    37      FB      38 FE    FE OF    CA 0000  C3 00A1
415      0212    37      FB      38 FE    FE OF    CA 0000  C3 00A1
416      0213    417     0214    C..OOOD  CP OFH   Z,000H  INPUT
417      0215    418     0216    C..OOOD  CP OFH   Z,000H  INPUT
418      0218    419     0218    C..OOOD  CP OFH   Z,000H  INPUT
419      021B    420     021B    C..OOOD  CP OFH   Z,000H  INPUT
421      021B    ED 5B 1005  DE,(MEM) ;Get the base address
422      0222    3A 1004  A,(NUMVEC) ;Save NUMVEC
423      0225    F5      AF      A,26H   ;Load the # of vectors
424      0225    F5      AF      A,(NUMVEC),A; And the address of MTEST
425      0226    3B 26      32 1004  LD H, MTEST ;And the address of MTEST
426      0228    3B 26      32 1004  LD (MEM), HL ;Save A in H
427      022B    21 0244  LD (MEM), HL ;Save A in H
428      022B    22 1005  POP AF
429      0231    F1      AF      H,A      ;Wait on next word
430      0232    67      INWATTI ;Set carry flag
431      0233    37      SCF    ;Enable interrupts
432      0234    37      EI     C..OOOE ;Wait on interrupt
433      0234    37      EI     C..OOOE ;Wait on interrupt
434      0235    38 FE    PUSH AF
435      0235    38 FE    LD A,H   ;A,H
436      0238    7C      LD (MEM), DE ;Restore display
437      0239    ED 53 1005  LD (NUMVEC), A; 32 1004
438      023D    32 1004  POP AF
439      0240    0241    F1      AF      SKLP   ;And go back
440      0241    C3 00A5

Reset Command
471      02B8    64 0C    66 0C  SUBTBL Reset Command
472      02BC    64 0A    65 0A  INWATTI ;Set carry flag
473      02C0    68 08    6A 08  ;Enable interrupts
474      02C4    6A 08    6A 0A  ;Wait on interrupt
475      02C8    6A 0A    68 0C  ;Is it the key?
476      02CC    68 0C    6A 0C  ;If so, RESET
477      02D0    68 0C    67 0C  ;If not, go back
478      02D4    6F 0C    67 0C  ;Small T
479      02D8    6C 0C    70 0C  ;Small T

Test Command
421      021B    ED 5B 1005  TEST:  SUBTBL Test Command
422      0222    3A 1004  ID DE,(MEM) ;Get the base address
423      0225    F5      PUSH A,(NUMVEC) ;Save NUMVEC
424      0225    F5      AF      A,26H   ;Load the # of vectors
425      0226    3B 26      32 1004  LD H, MTEST ;And the address of MTEST
426      0228    3B 26      32 1004  LD (MEM), HL ;Save A in H
427      022B    21 0244  LD (MEM), HL ;Save A in H
428      022B    22 1005  POP AF
429      0231    F1      AF      H,A      ;Wait on next word
430      0232    67      INWATTI ;Set carry flag
431      0233    37      SCF    ;Enable interrupts
432      0234    37      EI     C..OOOE ;Wait on interrupt
433      0234    37      EI     C..OOOE ;Wait on interrupt
434      0235    38 FE    PUSH AF
435      0235    38 FE    LD A,H   ;A,H
436      0238    7C      LD (MEM), DE ;Restore display
437      0239    ED 53 1005  LD (NUMVEC), A; 32 1004
438      023D    32 1004  POP AF
439      0240    0241    F1      AF      SKLP   ;And go back
440      0241    C3 00A5

Display Test Pattern
441      0244    00 00  FF 00  MTEST:  SUBTBL Display Test Pattern
442      0248    FF 00  FF 00  DB 00H, COH, OFPH, COH ;Large square
443      024C    FF 00  FF 00  DB 00H, COH, OFPH, OFPH
444      0250    00 00  FF 00  DB 00H, COH, COH, COH
445      0254    00 00  FF 00  DB 00H, COH, OFPH, OFPH ;Diagonals
446      0258    FF 00  FF 00  DB 00H, COH, COH, OFPH
447      025C    80  FF  80  00  DB 00H, OFPH, 00H, 00H ;Crosshairs
448      0260    FF 80  00  80  DB 00H, COH, 00H, COH ;Small box
449      0264    40 40  CO  CO  DB 00H, COH, COH, COH
450      0268    40 40  CO  CO  DB 00H, COH, COH, COH
451      026C    00  CO  CO  DB 00H, 00H, 040H, 040H ;Large T
452      0270    CO 40  40  40  DB 20H, 08H, 20H, 10H ;Large T
453      0274    20 08  20  10  DB 20H, 08H, 20H, 10H ;Large E
454      0278    10 10  24  10  DB 28H, 08H, 28H, 10H ;Large E
455      027C    28 08  28  10  DB 28H, 08H, 28H, 10H ;Large E
456      0280    28 08  2C  08  DB 28H, 08H, 2C, 08 ;Large S
457      0284    28 10  2C  10  DB 28H, 08H, 2C, 10H ;Large S
458      0288    28 0C  2A  0C  DB 28H, 08H, 34H, 0C ;Large S
459      028C    30 08  34  08  DB 34H, 08H, 34H, 0C
460      0290    34 08  34  0C  DB 34H, 08H, 34H, 0C
461      0294    34 0C  30 0C  DB 34H, 0C, 30H, 0C
462      0298    30 0C  30 10  DB 30H, 0C, 30H, 10H ;Large T
463      029C    30 10  34  10  DB 30H, 0C, 34H, 10H ;Large T
464      02A0    3C 08  3C  10  DB 33H, 0C, 34H, 10H ;Large T
465      02A4    38 10  40  10  DB 36H, 08H, 40H, 10H ;Small T
466      02B8    60 08  60  0C  DB 52H, 0C, 62H, 0C ;Small E
467      02AC    58 0C  62  0C  DB 64H, 08H, 64H, 0C ;Small E
468      02B0    64 08  64  0C  DB 64H, 08H, 66H, 0C ;Small E
479      02B4    64 08  66  08  DB 64H, 08H, 66H, 0C ;Small E

Macros And Symbols
Macros:
INWAITI
Symbols:
.0000  0090  ..0001  00A3  ..0002  COBA
.0004  012F  ..0005  0133  ..0006  0137
.0008  0140  ..0009  0166  ..0008  0168
.000C  0175  ..000D  0175  ..000E  0235
ALL   1FF7  CLEAR  010B  DECR  0207
DISP  ODDD  DRAW  0122  FIRST  0195
FIND1

```

```

GETCHR 02DC      HERE      0140      INIT      0000      INPUT    00A1
INRPT 0066      INPPTV    07FE      JTABLE   0708      LOOP    0143
MEM   1005      MODP     00B8      MTEST   0244      NORIND  0180
NOMORE 0083      NORMOVE  01D0      NOPE    01BC      NORICOM 0009
NUMV1 1000      NUMV2    1001      NUMV3    1002      NUMV4  1003
NUMV5C 1004      OK       011B      PAGE0   1007      PAGE1  1403
PAGE2 17FF      PAGE3    1BFB      REST    0212      SKLP    0045
PAGE2 17FF      TESTER   021E      UNDRAW  015C      WELL
TABLE 0700

```

No Fatal error(s)

Listing 2: The BASIC program LCIRCLE, for the TRS-80, used to create photo 2.

```

10 REM LCIRCLE BY BILLY GARRETT
20 DEFINT P,I,K,J,X,Y
30 DIM X(25),Y(25)
40 B=710/113
50 C1=255/2:C=C1
60 INPUT "INPUT NUMBER OF POINTS ON CIRCLE (3-23)";J
70 M=B/J:I=J-1
80 IF J>23 OR J<3 GOTO 60
90 INPUT "DRAW OR UNDRAW (D OR U)";SS
100 IF SS="D" THEN COM=4:GOT0130
110 IF SS="U" THEN COM=5:GOT0160
120 GOTO 90
130 INPUT "DO YOU WANT TO CLEAR THE PAGE FIRST (Y OR N)";A$
140 IF A$="Y" THEN OUT0 3:GOT0160
150 IF A$<>"N" GOTO 130
160 INPUT "WOULD YOU LIKE TO CHANGE THE RADIUS (10-127.5)";C
170 IF C>127.5 THEN EN160
180 FOR P=0 TO :D=M*P:X(P)=C*(COS(D)+1)+C1-C:NEXT P
190 FOR I=1 TO J1:FORK=I+1 TO J
200 OUT0,COM:GOSUB250:OUT0,X(I):OUT0,Y(I):OUT0,X(K):OUT0,Y(K):NEXT K,I
210 INPUT "ALL DONE. DO YOU WANT TO DO IT AGAIN (Y OR N)";A$
220 IF A$="N" END
230 IF A$="Y" GOTO 60
240 GOTO 210
250 IF INP(0)<12860 TO 250 ELSE RETURN

```

Listing 3: BASIC programs used to create images in photo 11.

(3a)

```

10 REM GRID BY BILLY GARRETT
20 INPUT "ENTER STEP RATE (1-254)";S
30 IF S<2 OR S>254 THEN 20
40 INPUT "DRAW OR UNDRAW";A$:
50 IF A$="D" THEN C=0 : GOT070
60 IF A$="U" THEN C=5 : GOT090
70 INPUT "CLEAR PAGE (Y OR N)";A$:
80 IF A$="Y" THEN OUT0,3
90 FOR A=0 TO 255 STEP S

```

The Sinclair Expanders

TIMEX 1000, ZX-81 (80)

8-Port I/O
Interfaces up to 8 one-byte ports
Accepts 16K RAM
10 \$89

ADDA
2-channels A/D (0-5V)
2-channels D/A (0-5V, 20mA)
ADDA \$89

Beeper (Clock / Switch)
m sec to years, three 16-bit counters, (reads on fly), 32KHz crystal, optically isolated input; programmable frequency tone generator...

BCS \$79


\$5 handling charge on all orders

ORDER TOLL FREE:
800-227-1617
operator 641
(CA, 800-772-3545
operator 641)

Box 1140
2000 Center Street
Berkeley, CA 94704

micro developments

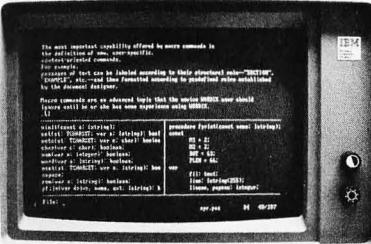Edix + Wordix has word processing features that our competitors are still dreaming about . . .



\$390 buys the whole dream.

Edix Editing Features
Up to 4 screen windows
Up to 12 file buffers
Top-to-bottom and side-to-side scrolling.
Regular expression searching and translating
Intra- and inter-buffer moving and copying
Online help
Online tutorial
Call or write for our brochure.

Wordix Formatting Features
Auto footnotes
Auto table of contents
Auto hyphenation
Multi-line headers and footers
Multi-column layout
Powerful macros
Data file access

Requires 128K IBM PC
Edix alone: \$195

EMERGING
TECHNOLOGY

Box 154 Louisville, Colorado 80027 303 447-9495

TM Trademark of Emerging Technology Consultants, Inc.


```

90 GOSUB130:OUT0,C:OUT0,B:OUT0,A:OUT0,B:OUT0,A:OUT0,B
100 GOSUB140:OUT0,C:GOSUB140:OUT0,A:OUT0,0:OUT0,A:OUT0,255
110 GOSUB140:OUT0,C:GOSUB140:OUT0,0:OUT0,A:OUT0,255:OUT0,A
120 NEXT A
130 GOTO 20
140 IF INP(0)<128 THEN 140 ELSE RETURN
(3b)
10 REM SPHERE BY BILLY GARRETT
20 DEFINT J,I,C,X,Y
30 DIM X(255),Y(255)
40 B=710/113
50 C=255/2
60 INPUT"INPUT NUMBER OF POINTS ON CIRCLE (3-254)";J
70 IF J>254 OR J<3 GOTO 60
80 INPUT"SCAN OR DRAW ONCE (S OR D)";P$
90 IF P$="S" S=5 :GOTO120
100 IF P$="D" S=4:GOTO120
110 GOTO80
120 N=B/J
130 FOR I=0TOJ:D=M*T:P:X(P)=C*(SIN(D)+1):Y(P)=C*(SIN(D)+1):NEXT P
140 INPUT"DO YOU WISH TO CLEAR THE DISPLAY (Y)";A:$:IFA$="Y":OUT0,3
150 IF S=5 THEN 180
160 FOR I=0TOJ-1:OUT0,4:OUT0,128:OUT0,X(I):OUT0,Y(I):NEXT I
170 GOTO 190
180 FOR I=0TOJ-1:OUT0,6:OUT0,4:OUT0,128:OUT0,X(I):OUT0,Y(I):NEXT I:GOT0180
190 INPUT"ALL DONE. DO YOU WANT TO DO IT AGAIN (Y OR N)";A:$
200 IF A$="N":END
210 IFA$="Y" GOTO 60
220 GOTO 190
(3c)
10 REM COCENTER BY BILLY GARRETT
20 DEFINT J,I,X,Y
30 DIM X(255),Y(255)
40 B=710/113
50 C1=255/2
60 INPUT"CLEAR PAGE (Y)";Y$:IF Y$="Y":OUT0,3
70 INPUT"INPUT NUMBER OF POINTS ON CIRCLES, AND NUMBER OF CIRCLES TO DRAW";J,N
80 IF J*N>255 GOTO 70
90 M=B/J
100 FOR C2=C1 TO 10 STEP -127.5/N
110 FOR P=0TOJ:D=M*T:P:X(P)=C2*(COS(D)+1)+C1-C2*Y(P)=C2*(SIN(D)+1)+C1-C2:NEXT P
120 FOR I=0TOJ-1:OUT0,4:OUT0,X(I):OUT0,Y(I):OUT0,X(I+1):OUT0,Y(I+1):NEXT I
130 NEXTC2
140 INPUT"ALL DONE. DO YOU WANT TO DO IT AGAIN (Y OR N)";A:$
150 IF A$="N":END
160 IFA$="Y" GOTO 40
170 GOTO 140
(3d)
10 REM BOXES BY BILLY GARRETT
20 DEFINT G,C,A
30 FOR G=64 TO 2 STEP-1
40 FOR C=4 TO 5
50 FOR A=0 TO 127 STEP 6
60 B=255-A
70 GOSUB130:OUT0,C:OUT0,A:OUT0,B:OUT0,A:OUT0,B:OUT0,A
80 GOSUB130:OUT0,C:OUT0,B:OUT0,A:OUT0,B:OUT0,A
(3e)
10 REM HOURGLASS BY BILLY GARRETT
20 INPUT"ENTER STEP RATE (1-254)";S
30 DEFINT A
40 OUT0,3
50 FOR A=0 TO 254 STEP S
60 OUT0,4:OUT0,A:OUT0,0:OUT0,255-A:OUT0,255
70 NEXT
80 GOTO 20
(3f)
10 REM SOLIDSIN BY BILLY GARRETT
20 M=10/113
30 INPUT"STEP,CYCLE";Q,B
40 INPUT"DO YOU WISH TO CLEAR THE DISPLAY (Y)";A:$:IFA$="Y":OUT0,3
50 FOR A=1 TO 255 STEP 0
60 OUT0,4:OUT0,A:OUT0,127.5*(SIN(A*M/B)+1):OUT0,A:OUT0,0:NEXT
70 INPUT"DO YOU WANT TO TRY AGAIN (Y)";A:$:IF A$="Y" THEN 20 ELSE END
(3g)
10 REM SSINE BY BILLY GARRETT
20 DIM X(511)
30 M=355/113*2/255: C=127.5: B=1
40 FOR A=0 TO 511
50 X(A)=C*(SIN(A*M)+B)
60 NEXT A
70 INPUT"DO YOU WISH TO CLEAR THE DISPLAY (Y)";A:$:IFA$="Y":OUT0,3
80 INPUT"STEP RATE (1-254)";S
90 FOR A=0 TO 255 STEP 255/S
100 IF A+S>255 GOTO 120
110 OUT0,4:OUT0,A:OUT0,X(A):OUT0,A+S:OUT0,X(A+S)
120 NEXT A
130 GOTO 70
(3d)
10 REM STICKS BY BILLY GARRETT
20 DEFINT A,S,X
30 DIM X(514)
40 M=355/113*2/255
50 FOR A=0 TO 513
60 X(A)=127.5*(SIN(A*M)+1):NEXT A
70 PRINT"HERE WE GO!!"
80 FOR S=6 TO 256:OUT0,1:OUT0,S:OUT0,2:OUT0,S-1:OUT0,3
90 FOR A=0 TO 255 STEP 255/S
100 IF A+S > 255 THEN Q=510-(A+S) ELSE Q=A+S
110 OUT0,4:OUT0,X(A):OUT0,X(512-A):OUT0,Q:OUT0,X(A+S)
120 NEXT A,S


```

Listing 4: The BASIC program STICKS used to create photo 3.


(11a)

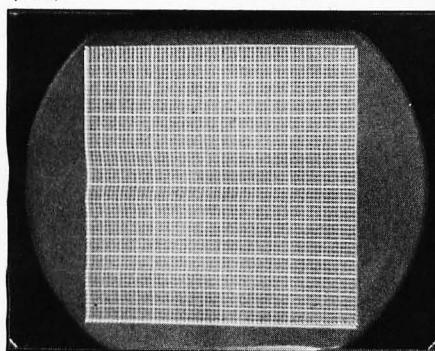


(11b)

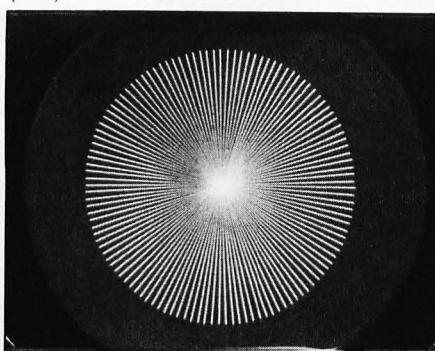


(11c)

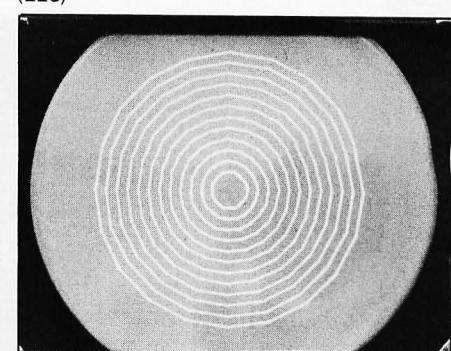


(11d)

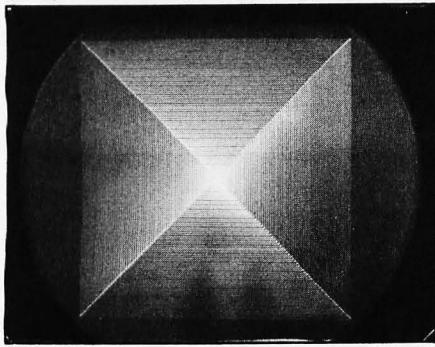

(11e)

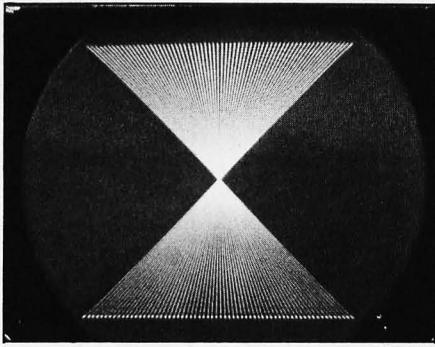

(11f)

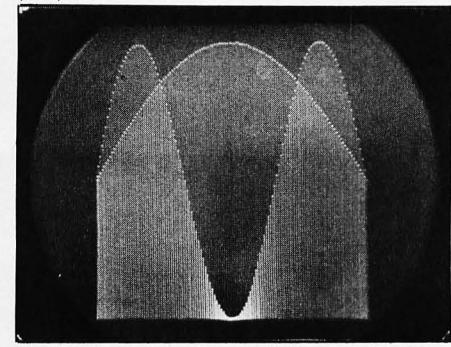

(11g)

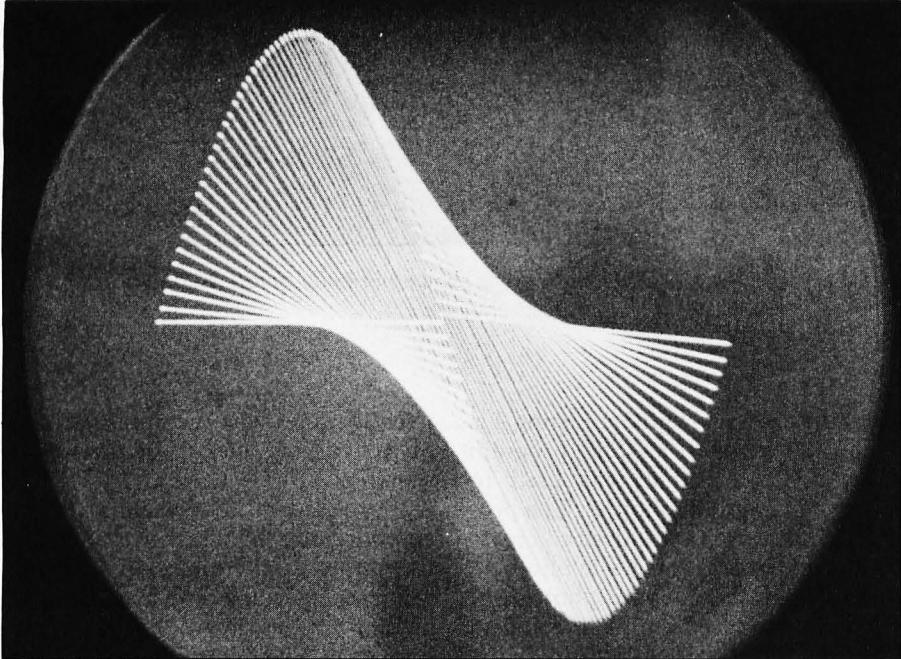


Photo 11: Examples of the elementary images that can be produced by Microvec. Each of these images was produced by a corresponding program in listing 3: photo 11a is a drawing produced by GRID, a BASIC program for the TRS-80 (see listing 3a); photo 11b was drawn by a program called SPHERE (listing 3b); photo 11c is the product of COCENTER (listing 3c); photo 11d is an image created by BOXES (listing 3d); photos 11e, 11f, and 11g were produced by HOURGLASS (listing 3e), SOLIDSIN (listing 3f), and SSINE (listing 3g), respectively.

Text continued from page 520:

that, adjust R18 and R26 to about 8.5 k Ω . Finally, adjust R10 to about 9 k Ω . Now, plug in the ICs, plug your board in, and hook the outputs up to your scope. Set the x and y channels of the scope to about 0.5 V/cm. Finally, turn on the power. If everything is

working properly, you should be able to see the board trying to display a few vectors on the screen. Eventually, these will look like the image in photo 8. If nothing happens, or you are having problems, go on to the next section, concerning Murphy's Law.


Once you obtain some kind of display, adjust the gain and zero controls of each channel until you get an output signal roughly ± 1 V centered about ground (see photo 10). Then, adjust the vector controller's slope controls until you see the diagonals intersect the middle. Next, vary the endpoint adjustment until the ends of the boxes just touch. You will have to play with the slope and endpoint adjustments for a while until the display looks right. Once you get your display looking like photo 8, you are almost finished. Next, increase the gain of each channel until the display begins to come apart. Then, back the gain down just a bit and adjust your oscilloscope so that the display fills the screen and the brightness is to your liking. If you get this far, you are doing very well.

Next, verify that all the commands work as described. A good check of the circuit board would be to run some of the programs in the later section of examples.


What to Do if Murphy's Law Is Enforced

You probably know the old saying, "If anything can go wrong, it will." This project will certainly be no exception. Refer to photos 4, 5, 6, and 7 if you are having problems. Read over the circuit description and make sure that the proper signals are at the given pins. For example:


(12a)

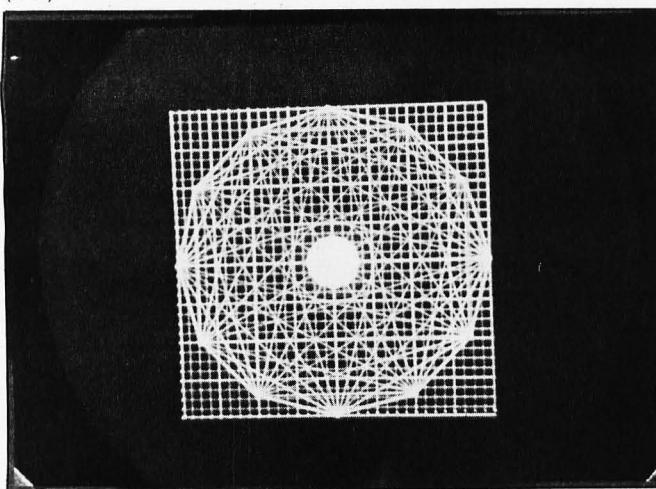

(12b)

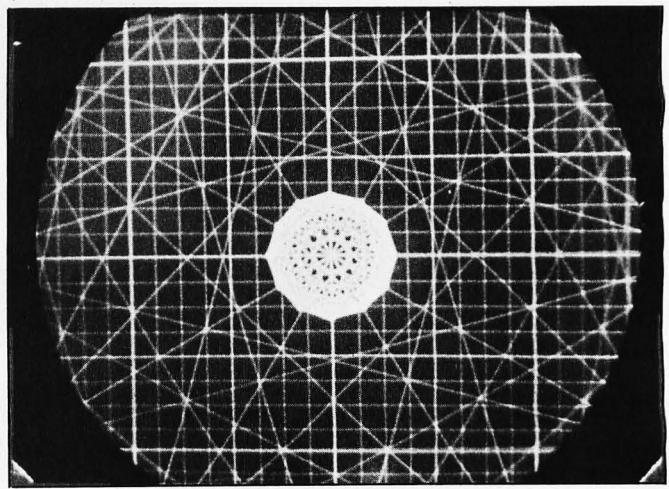

(12c)

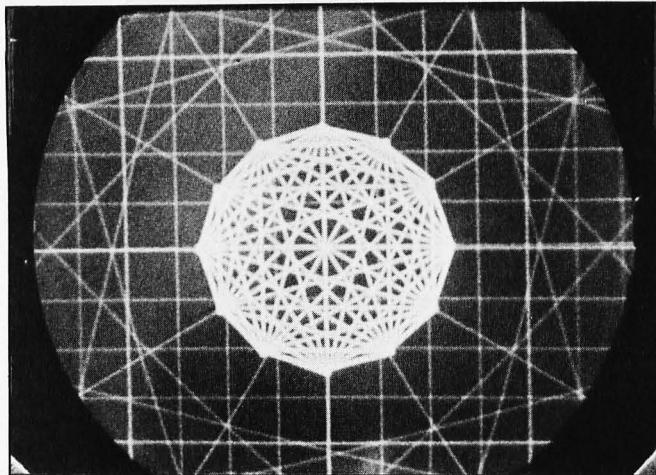

(12d)

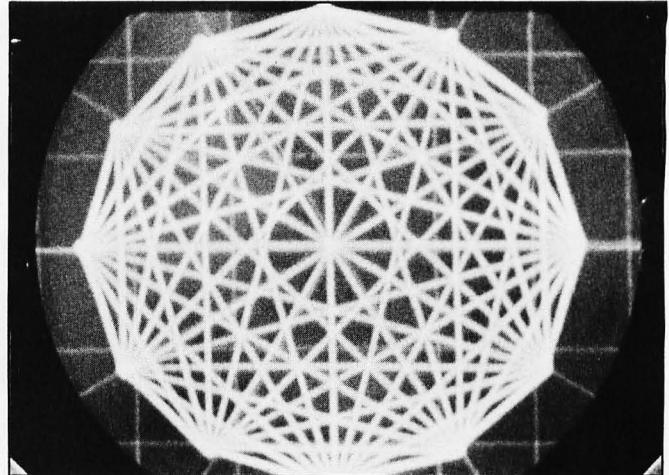


Photo 12: Using special features of the oscilloscope to alter images. Here, an image is shown normally (photo 12a) and with four-fold, sixteenfold, and hundredfold magnification (photos 12b, 12c, and 12d, respectively).

- If you are able to get a test pattern but it will not respond to commands, check to see that the data word is being strobed into the PIO when your processor does an I/O operation.
- If you suspect that the Z80 is running the wrong code, see if the NMI request pin is being pulsed as shown in photo 4.
- If the memory sections are not hooked up properly, you will not be getting the four short pulses on pin 15 of IC18, as is shown in photo 5.
- If the NMI pin of the Z80 does not remain high during and shortly after reset, the processor will almost certainly begin executing at the wrong address. Since R7 pulls the NMI line high during reset, make sure it is installed.

A Few Examples

Although the commands are fairly simple to understand, I have developed some examples that are both in-

structive and entertaining. Listing 2 is a TRS-80 Level II BASIC program called LCIRCLE that was used to draw the images in photo 2. The programs in listing 3 were used to create the corresponding images in photo 11 (e.g., listing 3b produced photo 11b, listing 3c produced photo 11c, and so on). The program STICKS, in listing 4, is the one that drew photo 3. The two parts of photo 1 are freehand "doodles" done with a program called SKETCH (not listed in this article).

Photos 12a through 12d show an interesting feature of the vector-graphics display. By simply increasing the gain on the oscilloscope, you can magnify the frame. The first photo is at the normal setting; the second is magnified by 4; the third is magnified by 16; and the last is magnified by 100 times. Notice that the little circle that was inside the larger circle is blown up so that it is larger than the original circle. All this

magnification was accomplished simply by varying the gain on the oscilloscope.

If you want to try animating a complicated scene, rather than trying to redraw each frame: first, put the same background in two different memory pages; then, by displaying one page while updating the next, you can swap the displayed pages back and forth to achieve the appearance of rapid motion. Your best teacher, though, will be experience.

Conclusion

This board is an exciting peripheral device for any computer. The first time you see these displays produced by your computer, you will not believe how sharp and detailed they are. Many creative uses for this display will be possible. I welcome suggestions or comments, but please enclose a SASE if you want a reply. Happy drawing! ■